




--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B. TECH.**  
**(SEM I) THEORY EXAMINATION 2020-21**  
**EMERGING DOMAIN IN ELECTRONICS ENGINEERING**

**Time: 3 Hours****Total Marks: 100****Note: 1.** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief.****2 x 10 = 20**

Q no.	Question	Marks	CO
a.	What do you mean by the term doping? Why it is required?	2	1
b.	List any two advantages of modulation.	2	3
c.	Evaluate: $(637)_9 = (?)_5$	2	2
d.	Draw the VI characteristics of an ideal diode in forward and reverse bias conditions.	2	2
e.	State two differences between microprocessor and microcontroller.	2	3
f.	Why bridge type full wave rectifier is preferred over center tapped full wave rectifier. State two reasons.	2	1
g.	State two differences between FET and BJT.	2	4
h.	Differentiate between avalanche and zener breakdown.	2	1
i.	Find 1's and 2's complement of : 1101001	2	2
j.	State the basic difference between Bluetooth and Wi-Fi technology.	2	2

**SECTION B****2. Attempt any three of the following:**

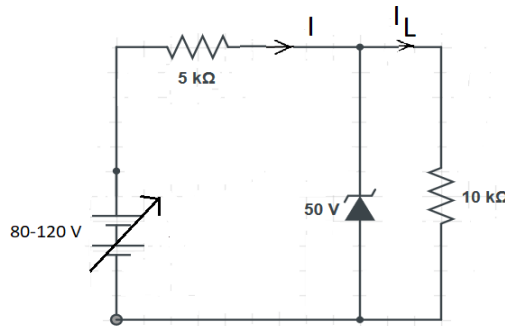Q no.	Question	Marks	CO
a.	(i) With help of neat circuit diagrams, explain the working of a full wave bridge rectifier. (ii) Define the term ripple factor. What is the value of the ripple factor for a half wave rectifier and a full wave rectifier?	6+4	3
b.	(i) With help of a neat diagram, explain the working of a voltage doubler circuit. (ii) Write a short note on varactor diode.	6+4	3
c.	For the circuit shown below, determine the value of maximum and minimum zener diode current.  	10	4
d.	(i) What are liquid crystal displays? Explain their working with help of a neat diagram. (ii) Determine the output waveform of the following circuit,	3+7	4



PAPER ID-311472

Roll  
No:

Printed Pages:  
PAGE 1 of 3  
Subject Code:  
KEC101T

Poori Padhai

Roll  
No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

e.	<p>(i) Determine the output waveform of the following circuit, by presenting all the necessary calculations which have been done to determine this output.</p> <p>(ii) Derive the relationship between current amplification factor for Common Emitter and Common Base configuration of a bipolar junction transistor.</p>	6+4	5

## SECTION C

3. Attempt any *one* part of the following:

Q no.	Question	Marks	CO
a.	Describe the construction of a npn bipolar junction transistor. Draw well labeled input and output characteristics of a npn transistor in Common Emitter Configuration. Also mark all the regions of operation	3+5+2	4
b.	Give the basic difference between an enhancement and depletion type MOSFET. Discuss the construction of a n channel depletion type MOSFET. Also draw its transfer and drain characteristics.	2+4+4	3

4. Attempt any *one* part of the following:

Q no.	Question	Marks	CO
a.	<p>(i) What is an operational amplifier? Draw its block diagram. Write the characteristics of an ideal operational amplifier.</p> <p>(ii) With help of the circuit diagram, explain the working of OPAMP as differentiator.</p>	5+5	3
b.	<p>(i) What do you mean by IOT? Discuss its various components.</p> <p>(ii) Define the following terms: (1) CMRR (2) Peak Inverse Voltage</p>	5+5	3

5. Attempt any *one* part of the following:

Q no.	Question	Marks	CO
a.	<p>Simplify the following function using K map</p> $F(A, B, C, D) = \sum(1, 3, 4, 5, 6, 7, 9, 11, 13, 15)$ <p>Also implement the simplified function using basic gates only.</p>	6+4	4



b.	By showing all the calculations, do as directed: (i) For a boolean function of 4 variables, $\Sigma(3,7,11,14,15) = \Pi(?)$	10	2
----	--	----	---

Poori Padhai

Roll  
No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

(ii) $(110110.011)_2 = (?)_{16}$		
(iii) $(231.36)_{10} = (?)_2$		
(iv) $(11011.10)_2 = (?)_{10}$		
(v) $(534)_8 = (?)_{10}$		

**6. Attempt any one part of the following:**

Q no.	Question	Marks	CO
a.	(i) What do you mean by amplitude modulation? Explain with help of proper waveforms. (ii) AM radio transmitter radiates 6 KW power when modulation percentage is 70 %. Determine the carrier power.	5+5	4
b.	(i) Write a short note on satellite communication system. (ii) Differentiate between CDMA and GSM?	5+5	3

**7. Attempt any one part of the following:**

Q no.	Question	Marks	CO
a.	(i) What are universal gates? Why are they called so? (ii) Implement XOR gate using NAND gate only.	5+5	2
b.	Determine the output for the following circuits:  (i) <div data-bbox="443 1137 1093 1579" data-label="Diagram"> </div> (ii) <div data-bbox="542 1653 1018 2083" data-label="Diagram"> </div>	5+5	4



PAPER ID-311472	Roll No:		
-----------------	-------------	--	--

XXXXXXXXXXXXXXXXXXXXXXXXXXXX

Poori Padhai