

**B. TECH.**  
**(SEM I) THEORY EXAMINATION 2018-19**  
**BASICS ELECTRONICS**

Time: 3 Hours

Total Marks: 70

**Note:** 1. Attempt all Sections. If require any missing data; then choose suitably.

**SECTION A**

1. Attempt *all* questions in brief.

2 x 7 = 14

- a) What is a ripple factor? Explain
- b) What is punch through effect?
- c) write advantages of digital voltmeter
- d) What is positive clamper and negative clamper?
- e) Define amplitude modulation.
- f) Explain why an ordinary transistor is called bipolar?
- g) Write the properties of an ideal op-amp

**SECTION B**

2. Attempt any *three* of the following

7 x 3 = 21



- a) Explain the operation of biased clipper and combination clipper
- b) Draw a self-biased circuit and derive an expression for stability factor.
- c) What is the difference between a CRT and CRO? Draw a neat block diagram of general purpose CRO and explain function of each block
- d) Draw a circuit diagram of inverting and non-inverting amplifier and the expression for output voltage.
- e) Write the advantages and disadvantages of a digital communication system.

**SECTION C**

3. Attempt any *one* part of the following:

7 x 1 = 7

- a) Explain how a barrier potential is developed at the P-N junction.
- b) Draw the output waveform for the circuit for the circuit of given figure

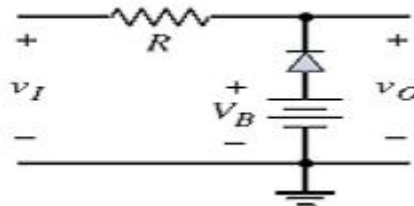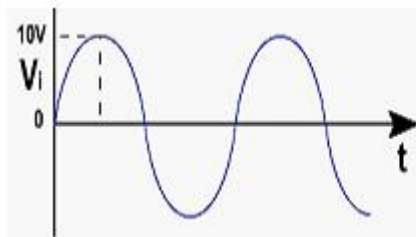4. Attempt any *one* part of the following:


7 x 1 = 7

- a) Explain the non-inverting summing amplifier with circuit diagram.
- b) With the help of a block diagram, explain the operation of a digital voltmeter.

5. Attempt any *one* part of the following:

7 x 1 = 7

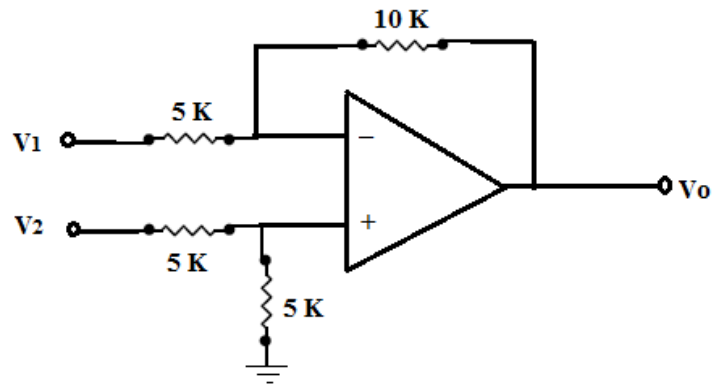- a) Write short notes on the following: Electrostatic focusing, measurement of phase angle by CRO.
- b) Find the output voltage of the Op-Amp circuit shown in figure, where  $V_1 = 10$  volt,  $V_2 = 5$  volt.



6. **Attempt any *one* part of the following:** **7 x 1 = 7**
- Explain the functioning of a buffer amplifier.
  - Explain the difference between baseband transmissions and pass band transmission.
7. **Attempt any *one* part of the following:** **7 x 1 = 7**
- Draw a simple circuit of a common collector amplifier and explain its operation.
  - The antenna current of an Am transmitter is 8 Amperes when only the carrier is sent, but it increases to 8.93 Amperes, when the carrier is modulated by a single sine wave. Find percentage modulation. Determine the antenna current when the percent of modulation changes to 0.8.